

Post-Lab: Burglar Alarm Circuit Questions

Answer the following questions in the space provided.

Summarize your observations after creating your working burglar alarm circuit.

How did your circuit diagram of the burglar alarm compare to your pre-lab schematic diagram. Be specific.
