

Lab: Burglar Alarm Circuit

In the space provided below, create a drawing of your burglar alarm circuit. Include all circuit parts as well as label the positive and negative end of the battery and color the buzzer's red and black wires.

Remember: A circuit diagram is a graphical representation of an electrical circuit.

Diagram of your circuit

